



**PANIMALAR INSTITUTE OF TECHNOLOGY  
(JAISAKTHI EDUCATIONAL TRUST)**

**DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING  
ACCREDITED BY NATIONAL BOARD OF ACCREDITATION  
MULTIPLE CHOICE QUESTIONS – UNIT I**

**Roll Number** :  
**Register Number** :  
**Subject code / Name** : CS8352 / Digital Principles and System Design  
**Year / Sem** : II / III  
**Date** :  
**Duration** : 40 minutes

1. The binary number 10101 is equivalent to decimal number .....

- a. 19
- b. 12
- c. 27
- d. 21

2. The universal gate is .....

- a. NAND gate
- b. OR gate
- c. AND gate
- d. None of the above

3. The inverter is .....

- a. NOT gate
- b. OR gate
- c. AND gate
- d. None of the above

4. The inputs of a NAND gate are connected together. The resulting circuit is .....

- a. OR gate
- b. AND gate
- c. NOT gate
- d. None of the above

5. The NOR gate is OR gate followed by .....

- a. AND gate
- b. NAND gate
- c. NOT gate
- d. None of the above

6. The NAND gate is AND gate followed by .....

- a. NOT gate
- b. OR gate
- c. AND gate
- d. None of the above

7. Digital circuit can be made by the repeated use of .....

- a. OR gates
- b. NOT gates
- c. NAND gates
- d. None of the above

8. The only function of NOT gate is to .....

- a. Stop signal
- b. Invert input signal
- c. Act as a universal gate
- d. None of the above

9. When an input signal 1 is applied to a NOT gate, the output is .....

- a. 0
- b. 1
- c. Either 0 & 1
- d. None of the above

10. In Boolean algebra, the bar sign (-) indicates .....

- a. OR operation
- b. AND operation
- c. NOT operation
- d. None of the above

11. 2's complement of binary number 0101 is .....

- a. 1011
- b. 1111

- c. 1101
- d. 1110

12. An OR gate has 4 inputs. One input is high and the other three are low. The output is .....

- a. Low
- b. High
- c. alternately high and low
- d. may be high or low depending on relative magnitude of inputs

13. Decimal number 10 is equal to binary number .....

- a. 1110
- b. 1010
- c. 1001
- d. 1000


14. Both OR and AND gates can have only two inputs.

- a. True
- b. False

15. In 2's complement representation the number 11100101 represents the decimal number

- a. +37
- b. -31
- c. +27
- d. -27

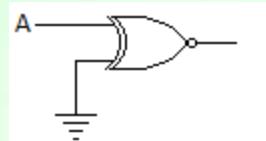16. For the gate in the given figure the output will be .....



- a. 0
- b. 1
- c. A
- d.  $\bar{A}$

17. In the expression  $A + BC$ , the total number of minterms will be

- a. 2
- b. 3
- c. 4
- d. 5

18. The number of digits in octal system is .....

- a. 8
- b. 7
- c. 9
- d. 10

19. The expression  $Y = \pi M(0, 1, 3, 4)$  is .....

- a. POS
- b. SOP
- c. Hybrid
- d. none of these


20. Decimal 43 in hexadecimal is .....

- a. B2
- b. 2B
- c. 2B
- d. B2

21. Decimal 43 in BCD number system is .....

- a. 01000011
- b. 01000011
- c. 00110100
- d. 01000100

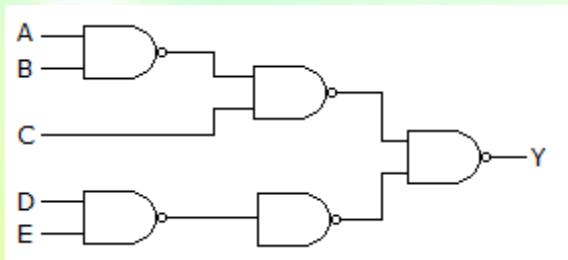22. The circuit of the given figure realizes the function .....



- 1.  $Y = (\bar{A} + \bar{B})C + \bar{D}\bar{E}$
- 2.  $Y = \bar{A} + \bar{B} + \bar{C} + \bar{D} + \bar{E}$
- 3.  $AB + C + DE$
- 4.  $AB + C(D + E)$

23. An AND gate has two inputs A and B and one inhibit input 3, Output is 1 if

- a.  $A = 1, B = 1, S = 1$
- b.  $A = 1, B = 1, S = 0$

- c. A = 1, B = 0, S = 1
- d. A = 1, B = 0, S = 0

24. The greatest negative number which can be stored in 8 bit computer using 2's complement arithmetic is .....

- a. -256
- b. -128
- c. -255
- d. -127

25.  $7BF_{16} = \underline{\hspace{2cm}}_2$

- a. 0111 1011 1110
- b. 0111 1011 1111
- c. 0111 1011 0111
- d. 0111 1011 0011